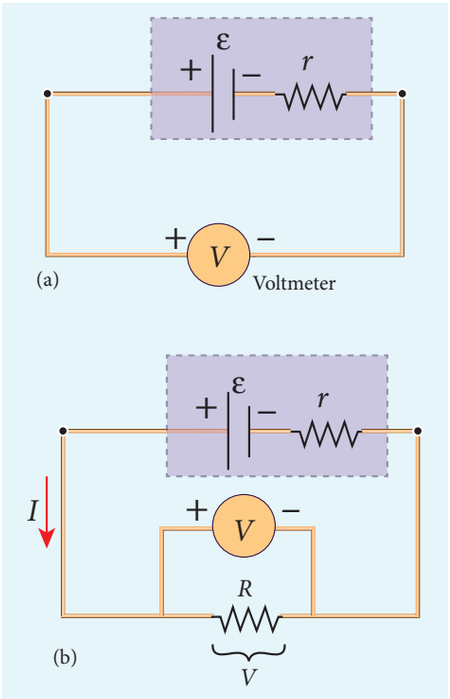


Figure 2.20 Internal resistance of the cell

R is equal to the potential difference across the cell (V) as shown in Figure 2.20(b).

The potential drop across the resistor R is

$$V = IR \qquad (2.35)$$

Due to internal resistance r of the cell, the voltmeter reads a value V, which is less than the emf of cell ε. It is because, certain amount of voltage (Ir) has dropped across the internal resistance r.

Then $V = \varepsilon - Ir$

$$Ir = \varepsilon - V \qquad (2.36)$$

Dividing equation (2.36) by equation (2.35), we get

$$\frac{Ir}{IR} = \frac{\varepsilon - V}{V}$$

$$r = \left[\frac{\varepsilon - V}{V}\right] R \qquad (2.37)$$

Since ε, V and R are known, internal resistance r can be determined. We can also find the total current that flows in the circuit.

Due to this internal resistance, the power delivered to the circuit is not equal to power rating mentioned in the battery. For a battery of emf ε, with an internal resistance r, the power delivered to the circuit of resistance R is given by

$P = I\varepsilon = I\,(V + Ir)$ (from equation 2.36)

Here V is the voltage drop across the resistance R and it is equal to IR.

Therefore, $P = I\,(IR + Ir)$

$$P = I^2 R + I^2 r \qquad (2.38)$$

Here I^2r is the power delivered to the internal resistance and I^2R is the power delivered to the electrical device (here it is the resistance R). For a good battery, the internal resistance r is very small, then $I^2r << I^2R$ and almost entire power is delivered to the external resistance.

EXAMPLE 2.17

A battery has an emf of 12 V and connected to a resistor of 3 Ω. The current in the circuit is 3.93 A. Calculate (a) terminal voltage and the internal resistance of the battery (b) power delivered by the battery and power delivered to the resistor

Solution

The given values $I = 3.93$ A, $\varepsilon = 12$ V, $R = 3\ \Omega$

(a) The terminal voltage of the battery is equal to voltage drop across the resistor

$V = IR = 3.93 \times 3 = 11.79$ V

12th Physics_Vol-1_Unit 2_English Medium.indd 101 12-12-2022 17:24:03