A galvanometer is converted into an ammeter by connecting a low resistance in parallel with the galvanometer. This low resistance is called shunt resistance *S*. The scale is now calibrated in ampere and the range of ammeter depends on the values of the shunt resistance.

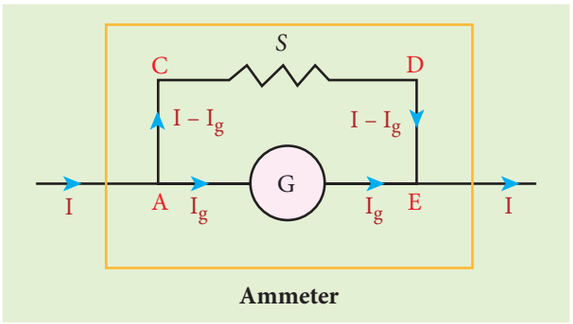


Figure 3.61 Shunt resistance connected in parallel

Let I be the current passing through the circuit as shown in Figure 3.61. When current I reaches the junction A, it divides into two components. Let I_g be the current passing through the galvanometer of resistance R_g through a path AGE and the remaining current $(I - I_g)$ passes along the path ACDE through shunt resistance S. The value of shunt resistance is so adjusted that current I_g produces full scale deflection in the galvanometer. The potential difference across galvanometer is same as the potential difference across shunt resistance.

$$V_{galvanometer} = V_{shunt}$$

$$\Rightarrow I_g R_g = (I - I_g) S$$

$$S = \frac{I_g}{(I - I_g)} R_g \text{ or}$$

$$I_g = \frac{S}{S + R_g} I$$

Since, the deflection in the galvanometer is proportional to the current passing through it,

$$\theta = \frac{1}{G} I_g \Rightarrow \theta \propto I_g \Rightarrow \theta \propto I \text{ So,}$$

the deflection produced in the galvanometer is a measure of the current I passing through the circuit.

Shunt resistance is connected in parallel to galvanometer. Therefore, resistance of ammeter (R_a) can be determined by computing the effective resistance, which is

$$\frac{1}{R_{eff}} = \frac{1}{R_g} + \frac{1}{S} \Rightarrow R_{eff} = \frac{R_g S}{R_g + S} = R_a$$

Since, the shunt resistance is a very low resistance and the ratio $\frac{S}{R_g}$ is also small. This means, R_a is also small, i.e., the resistance offered by the ammeter is small. So, when we connect ammeter in series, the ammeter will not change appreciably the current in the circuit. For an ideal ammeter, the resistance must be equal to zero. But in reality, the reading in ammeter is always less than the actual current in the circuit. Let I_{ideal} be the current measured by ideal ammeter and I_{actual} be the actual current in the circuit. Then, the percentage error in measuring a current through an ammeter is

$$\frac{\Delta I}{I} \times 100\% = \frac{I_{ideal} - I_{actual}}{I_{ideal}} \times 100\%$$

Key points

1. An ammeter is a low resistance instrument and it is always connected in series to the circuit
2. An ideal ammeter has zero resistance

12th Physics_Vol-1_Unit 3_English Medium.indd 184 23-12-2022 15:03:57