3. COMPARISON OF EMF OF TWO CELLS USING POTENTIOMETER

AIM

To compare the emf of the given two cells using a potentiometer.

APPARATUS REQUIRED

Battery eliminator, key, rheostat, DPDT switch, Lechlanche and Daniel cells, galvanometer, high resistance box, pencil jockey and connecting wires.


FORMULA

$$\frac{\varepsilon_1}{\varepsilon_2} = \frac{l_1}{l_2} \text{ (no unit)}$$

where, ε_1 and ε_2 are the emf of Lechlanche and Daniel cells respectively (V)

l_1 and l_2 are the balancing lengths for Lechlanche and Daniel cells respectively (cm)

CIRCUIT DIAGRAM

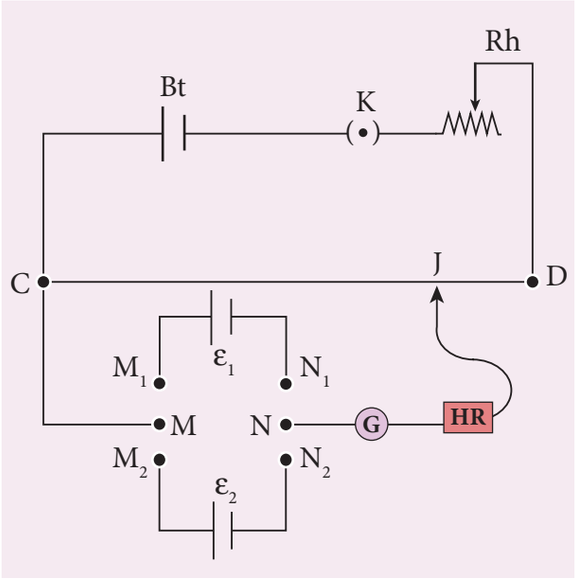

PROCEDURE

- The apparatus is arranged as shown in the circuit diagram.
- The primary circuit consisting of battery, key and rheostat is connected to the potentiometer in series.
- The positive poles of the cells are connected to terminals M_1 & M_2 and the negative poles to terminals N_1 & N_2 of the DPDT switch. The potentiometer is connected to the common terminals M and N as shown in the circuit.
- Using the two-way key, Lechlanche cell is included in the circuit. By sliding the jockey on the potentiometer wire, the balancing point is found and the corresponding balancing length is measured.
- Similarly, the balancing length is found by including Daniel cell in the circuit.
- The experiment is repeated for different sets of balancing lengths by adjusting the rheostat.
- From different values of l_1 and l_2, the ratio of emf of the two cells is calculated.

XII-Physics_Vol-1) PRACTICAL.indd 294 08-12-2022 11:00:34