OBSERVATION

Table: To find the ratio of emf of two cells

S.No	Balancing length for Lechlanche cell, l_1 (cm)	Balancing length for Daniel cell, l_2 (cm)	$\frac{\varepsilon_1}{\varepsilon_2} = \frac{l_1}{l_2}$
1			
2			
3			
4			
5			

Mean $\frac{\varepsilon_1}{\varepsilon_2} =$

CALCULATION

$$\frac{\varepsilon_1}{\varepsilon_2} = \frac{l_1}{l_2}$$

RESULT

Ratio of emf of the given two cells = _____ (no unit)

Note:

DPDT switch



Double Pole Double Throw (DPDT) switch is a 6-terminal key with a throw switch (metal handle) attached to the common terminals M and N. The two-given cells are connected to the pairs of terminals M_1 & M_2 and
N_1 & N_2. When the handle is thrown to one side, say M_1 & M_2, the cell that is connected to that pair of terminals is included with the primary circuit.

XII-Physics_Vol-1) PRACTICAL.indd 295 08-12-2022 11:00:34