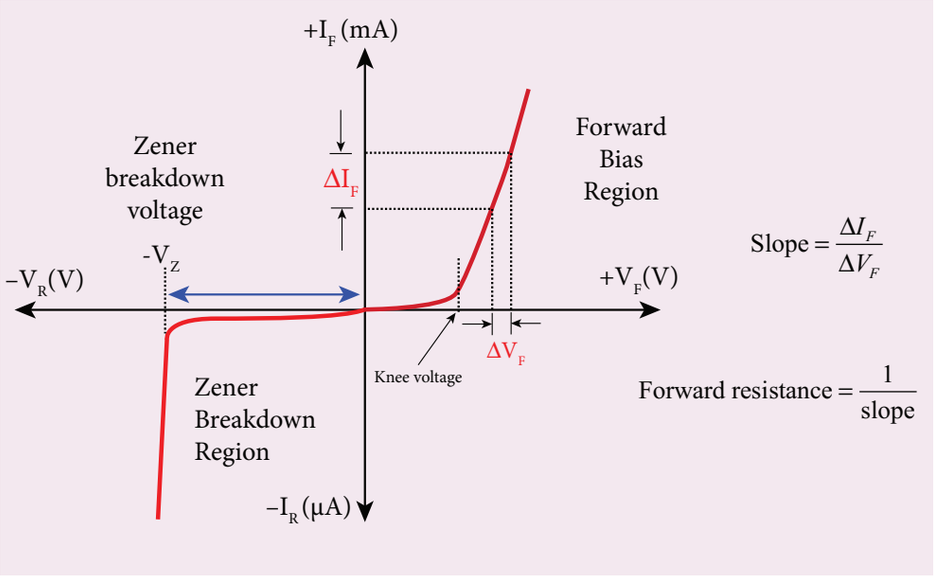


OBSERVATION

Table 1 Forward bias characteristic curve

S.No.	Forward bias voltage V_F (volt)	Forward bias current I_F (mA)

Table 2 Reverse bias characteristic curve

S.No.	Reverse bias voltage V_R (volt)	Reverse bias current I_R (mA)

CALCULATION

(i) Forward resistance R_F=

(ii) knee voltage =

(iii) The breakdown voltage of the Zener diode V_Z= ----V

XII-Physics_Vol-1) PRACTICAL.indd 308 08-12-2022 11:00:41