
S.No	V_{CE}=1V		V_{CE}=2V	
	I_B (μA)	I_C (mA)	I_B (μA)	I_C (mA)

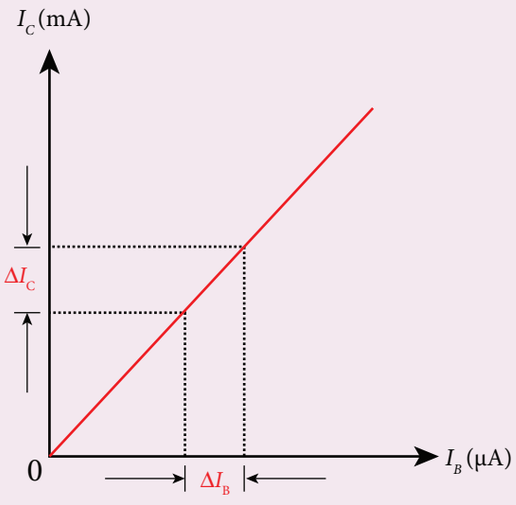

$$\text{Slope} = \frac{\Delta I_C}{\Delta I_B}$$

Current gain = slope

RESULT

i) The input, output and transfer characteristics of the NPN junction in common emitter mode are drawn.

ii) (a) Input impedance = _____Ω

(b) Output impedance = _____Ω

(c) Current gain β = ____(no unit)

XII-Physics_Vol-1) PRACTICAL.indd 313 08-12-2022 11:00:43