9. VERIFICATION OF TRUTH TABLES OF LOGIC GATES USING INTEGRATED CIRCUITS

AIM

To verify the truth tables of AND, OR, NOT, EX-OR, NAND and NOR gates using integrated circuits

COMPONENTS REQUIRED

AND gate (IC 7408), NOT gate (IC 7404), OR gate (IC 7432), NAND gate (IC 7400), NOR gate (IC 7402), X-OR gate (IC 7486), Power supply, Digital IC trainer kit, connecting wires.

BOOLEAN EXPRESSIONS

(i) AND gate $Y = A.B$

(ii) OR gate $Y = A+B$

(iii) NOT gate $Y = \overline{A}$

(iv) Ex OR gate $Y = \overline{A}B + A\overline{B}$

(v) NAND gate $Y = \overline{A.B}$

(vi) NOR gate $Y = \overline{A+B}$

CIRCUIT DIAGRAM

Pin Identification


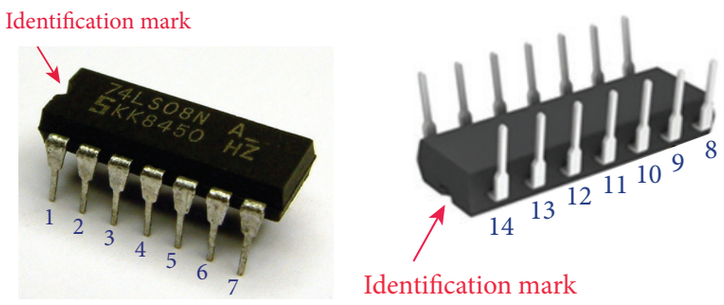


Figure (a) Integrated circuit

Note:

The chip must be inserted in the bread board in such a way that the identification mark should be on our left side. In this position, pin numbers are counted as marked in the picture above. Pin identification is the same for all chips that are mentioned below.


AND Gate:

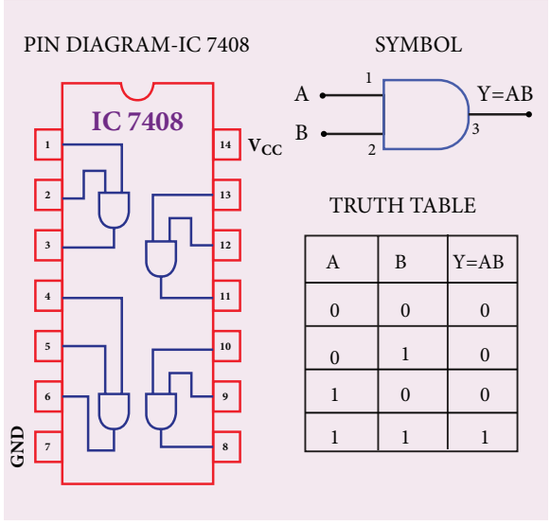

TRUTH TABLE

A	B	Y=AB
0	0	0
0	1	0
1	0	0
1	1	1

OR Gate:

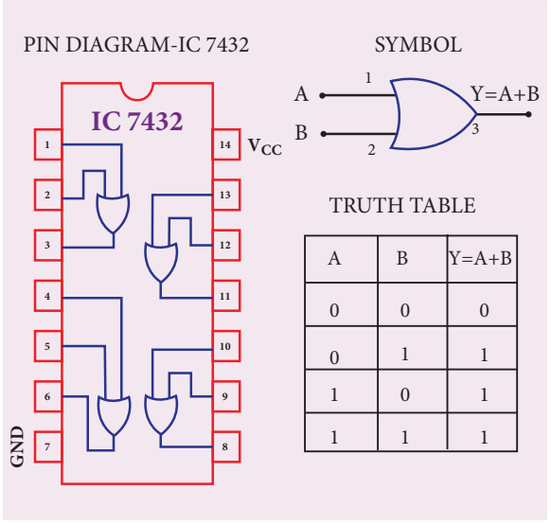

TRUTH TABLE

A	B	Y=A+B
0	0	0
0	1	1
1	0	1
1	1	1

XII-Physics_Vol-1) PRACTICAL.indd 314 08-12-2022 11:00:44