
4. State macroscopic form of Ohm's law.
5. What are ohmic and non ohmic devices?
6. Define electrical resistivity.
7. Define temperature coefficient of resistance.
8. What is superconductivity?
9. What is electric power and electric energy?
10. Define current density.
11. Derive the expression for power P=VI in electrical circuit.
12. Write down the various forms of expression for power in electrical circuit.
13. State Kirchhoff's current rule.
14. State Kirchhoff's voltage rule.
15. State the principle of potentiometer.
16. What do you mean by internal resistance of a cell?
17. State Joule's law of heating.
18. What is Seebeck effect?
19. What is Thomson effect?
20. What is Peltier effect?
21. State the applications of Seebeck effect.

III Long Answer Questions

1. Describe the microscopic model of current and obtain general form of Ohm's law
2. Obtain the macroscopic form of Ohm's law from its microscopic form and discuss its limitation.
3. Explain the equivalent resistance of a series and parallel resistor network
4. Explain the determination of the internal resistance of a cell using voltmeter.
5. State and explain Kirchhoff's rules.
6. Obtain the condition for bridge balance in Wheatstone's bridge.
7. Explain the determination of unknown resistance using meter bridge.
8. How the emf of two cells are compared using potentiometer?

IV Numerical problems

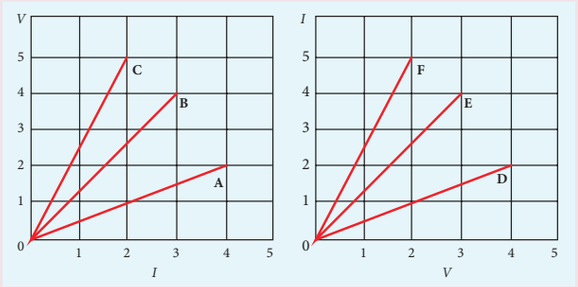1. The following graphs represent the current versus voltage and voltage versus current for the six conductors A,B,C,D,E and F. Which conductor has least resistance and which has maximum resistance?



Ans: Least: $R_F = 0.4\ \Omega$, maximum $R_C = 2.5\ \Omega$

2. Lightning is very good example of natural current. In typical lightning, there is 10^9 J energy transfer across the potential difference of 5×10^7 V during a time interval of 0.2 s.



UNIT-2(XII-Physics_Vol-1).indd 123 04-03-2019 11:02:01