
	P	Q	R	S
P removed	*	on	on	on
Q removed	on	*	on	off
R removed	off	off	*	off
S removed	on	off	on	*

Draw the circuit diagram for these bulbs.

Ans:

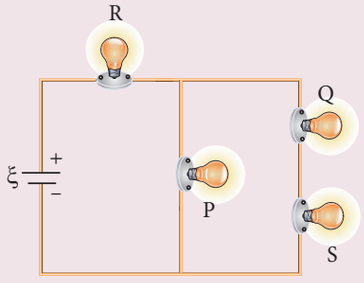

15. In a potentiometer arrangement, a cell of emf 1.25 V gives a balance point at 35 cm length of the wire. If the cell is replaced by another cell and the balance point shifts to 63 cm, what is the emf of the second cell?

Ans: emf of the second cell is 2.25 V

BOOKS FOR REFERENCE:

1. Douglas C.Giancoli, , "*Physics for Scientist &Engineers with Modern Physics*", Pearson Prentice Hall, Fourth edition
2. James Walker, *Physics*, Pearson- Addison Wesley publishers, Fourth edition
3. Tipler, Mosca, "*Physics for scientist and Engineers with Modern Physics*", Freeman and Company, sixth edition
4. Purcell, Morin, *Electricity and magnetism*, Cambridge university press, third edition
5. Serway and Jewett, "*Physics for Scientist and Engineers with Modern Physics*", Brook/Coole publishers, eighth edition
6. Tarasov and Tarasova, "*Questions and problems in School Physics*", Mir Publishers
7. H.C.Verma, "*Concepts of Physics Vol 2*, Bharthi Bhawan publishers
8. Eric Roger, *Physics for the Inquiring Mind*, Princeton University press