Table 2 To find the radius of the wire

Zero error =

Zero correction =

LC = 0.01 mm

| Sl.No. | PSR (mm) | HSC (div.) | Total Reading = PSR + (HSC × LC) (mm) | Corrected Reading = TR ± ZC (mm) |
|---|---|---|---|---|
| 1 | | | | |
| 2 | | | | |
| 3 | | | | |
| 4 | | | | |
| 5 | | | | |
| 6 | | | | |

Mean diameter 2r = ..... cm

Radius of the wire r = ..... cm

r = ..... m

## CALCULATION

(i) $\rho = \frac{X\pi r^2}{L}$ =

## RESULT

The specific resistance of the material of the given coil = _____(Ωm)

**Note:**

i) To check the circuit connections:

The meter bridge wire is touched near one end (say, end A) with jockey, galvanometer shows a deflection in any one direction. Now the other end (say, end B) is touched. If the galvanometer shows a deflection in the opposite direction, then the circuit connections are correct.

ii) The usage of high resistance (HR):

The galvanometer is a very sensitive device. If any high current flows through the galvanometer, its coil gets damaged. Therefore in order to protect the galvanometer, a high resistance (HR) is used. When HR is connected in series with the galvanometer, the current through it is reduced so that the galvanometer is protected. But the balancing length is not accurate.

iii) To find the accurate balancing length:

The HR is first included in the circuit (that is, the plug key in HR is removed), the approximate balancing length is found. Now HR is excluded in the circuit (that is, the plug key in HR is closed), then the accurate balancing length is found.



XII-Physics_Vol-1) PRACTICAL.indd 307 04-03-2019 11:06:38