
Note

NAND and NOR gates are known as universal gates because any other logic gate can be made from NAND or NOR gates.

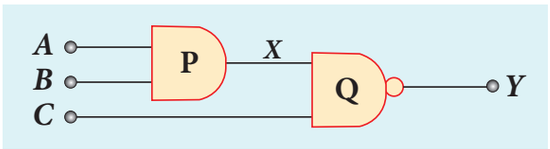EXAMPLE 10.9

What is the output Y in the following circuit, when all the three inputs A, B, and C are first 0 and then 1?




Solution

A	B	C	$X = A \cdot B$	$Y = \overline{X \cdot C}$
0	0	0	0	1
1	1	1	1	0

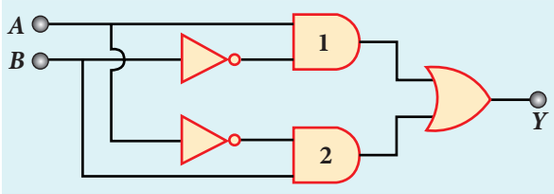EXAMPLE 10.10

In the combination of the following gates, write the Boolean equation for output Y in terms of inputs A and B.



Solution

The output at the 1st AND gate: $A\overline{B}$

The output at the 2nd AND gate: $\overline{A}\,B$

The output at the OR gate: $Y = A.\overline{B} + \overline{A}.B$

10.6 BOOLEAN ALGEBRA

Boolean Algebra is basically a choice between two options (i) yes or no (ii) high or low. These two options in Boolean algebra are represented by binary numbers 0 or 1. It is a concept that relates logic and mathematics which is a century old, made up by George Boole in 1854. Later the importance of Boolean algebra was realized in the design of computer circuits. Today we are in a digital world and most of the comforts that we experience is due to digitization with the foundation based on Boolean algebra.

Do You Know?

The concept of high (1) and low (0) is not a new one. In fact, it was applied in telephone switching circuits by Shannon in 1938.

Laws of Boolean Algebra

The NOT, OR and AND operations discussed in section 10.5.2 are the Boolean operations. The results of these operations can be summarised as:

Complement law

A	$Y = \overline{A}$
0	$Y = \overline{0} = 1$
1	$Y = \overline{1} = 0$

The complement law can be realised as $\overline{\overline{A}} = A$

XII_Physics_Vol-2_UNIT-10_Part 1_EM.indd 230 19-12-2022 16:39:18