
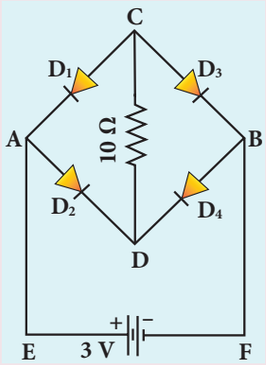


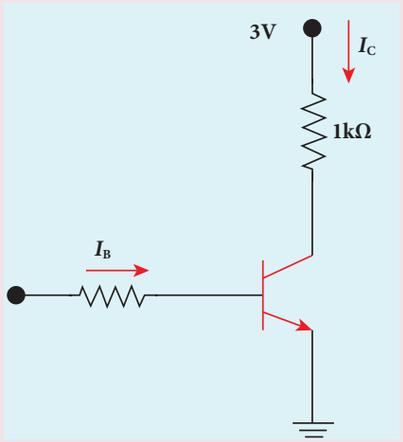
2. Four silicon diodes and a 10 Ω resistor are connected as shown in figure below. Each diode has a resistance of 1Ω. Find the current flows through the 10Ω resistor. [Ans: 0.13 A]



3. Assuming V_{CEsat} = 0.2 V and β = 50, find the minimum base current (I_B) required to drive the transistor given in the figure to saturation. [Ans: 56 μA]




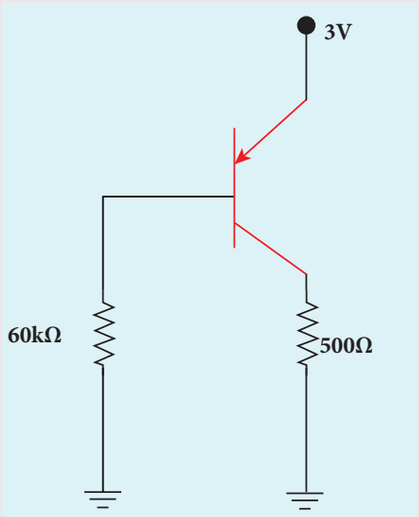4. In the circuit shown in the figure, the BJT has a current gain (β) of 50. For an emitter – base voltage V_{EB} = 600 mV, calculate the emitter – collector voltage V_{EC} (in volts). [Ans: 2 V]



5. Determine the current flowing through 3Ω and 4Ω resistors of the circuit given below. Assume that diodes D_1 and D_2 are ideal diodes.

[Ans: 0 and 2A]

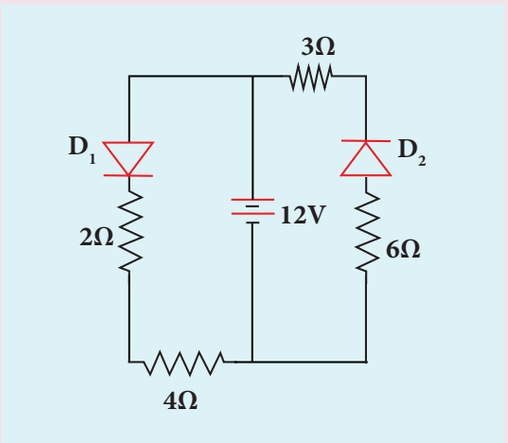

XII_Physics_Vol-2_UNIT-10_Part 2_EM.indd 249 04-03-2022 17:19:27