ICT CORNER

Electronics and Communication


In this activity you will be able to (i) Construct , manipulate and simulate the logic circuits. (ii) verify the truth tables of AND, OR, NOT, EX-OR, NAND and NOR gates

Topic: Logic gates


STEPS:

- Open the browser and type "circuitverse.org/simulator" in the address bar.
- Click 'Gates' tab from the circuit elements. Select the gate you want to verify and drag it in to the stage.
- Nodes in the logic gates are connected through wires. Wires can be drawn by dragging from the nodes with the help of mouse.
- Select 'input tool' from input tab. Drag and keep it as two inputs.
- Select 'output tool' or 'digital LED' from output tab. Drag and keep it as output.
- Verify the truth tables of AND, OR, NOT, EX-OR, NAND and NOR gates. You can verify De Morgan's first and second theorems.


Step1

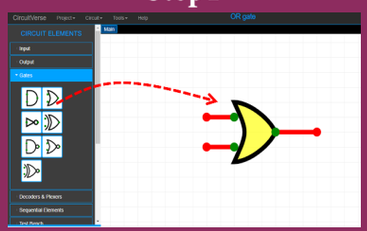


Step2

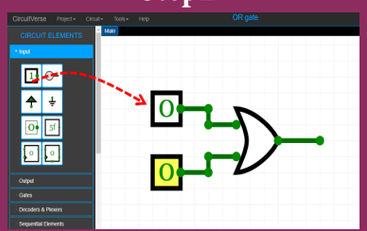

Step3

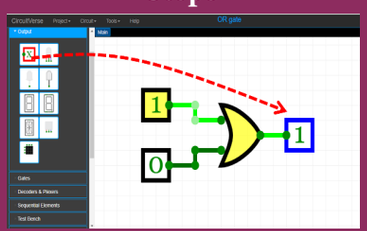

Step4

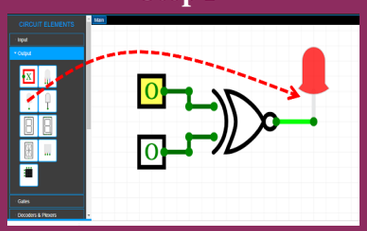

Note:

Login with the help of your mail id if you want to save your project in online.

URL:

https://circuitverse.org/simulator

* Pictures are indicative only.

* If browser requires, allow **Flash Player** or **Java Script** to load the page.

XII_Physics_Vol-2_UNIT-10_Part 2_EM.indd 252 04-03-2022 17:19:27